

EE 420

SEPT 18, 1974

LAB #1

EXPERIMENT IN PULSED TRANSMISSION LINES

PURPOSE: The purpose of this experiment is:

- 1) To demonstrate the traveling wave phenomenon in a transmission line and,
- 2) To demonstrate the reflections of such waves by various terminations on the line

GENERAL: Figure 1 illustrates the laboratory setup to be used. A long coaxial transmission line has been created by patching together all of the RG-8/U cables between the various laboratories on the third floor of Coover Hall, so that both ends of the line ("A" & "B" in figure 1) are available side by side in the Microwave Lab.

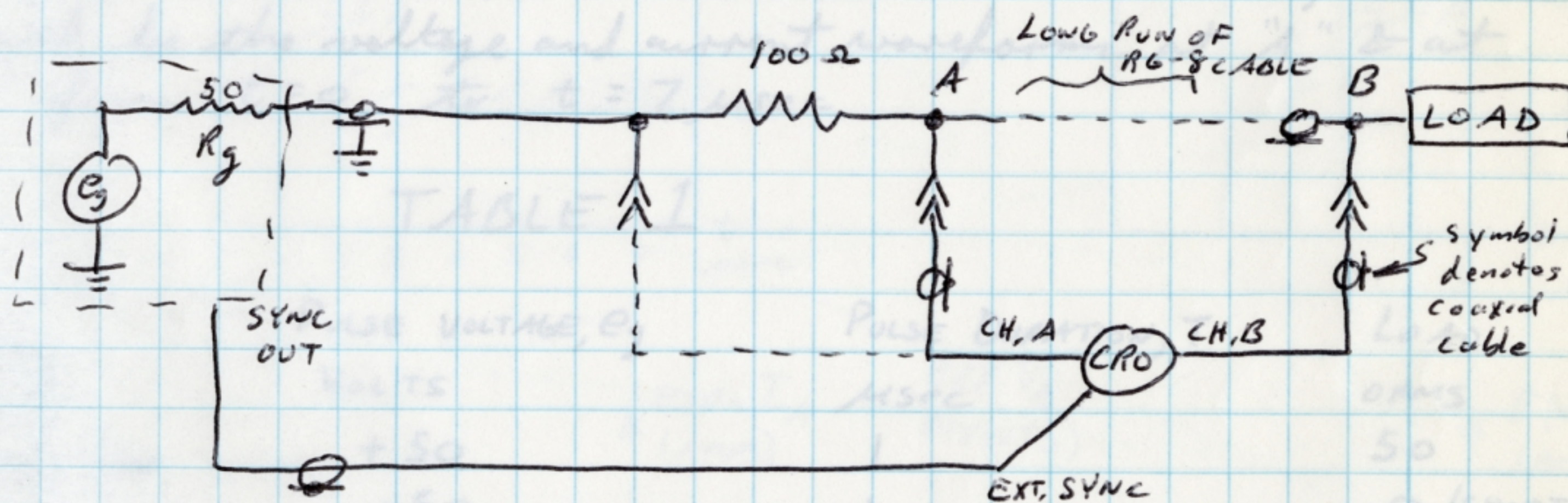


FIGURE 1

PRELIMINARY

1. Type RG-8/U cable has characteristic impedance $R_0 = 50.0 \Omega$ and a capacitance $C = 29.5 \text{ pF per foot}$. [This data obtained from Reference Data for Radio Engineers, 4th ed., page 608]

$$V = \frac{1}{\sqrt{LC}}$$

$$R_0 = \sqrt{\frac{L}{C}} \Rightarrow L = R_0^2 C$$

$$\therefore V = \frac{1}{R_0 C}$$

$$= \frac{1}{(50)(29.5 \cdot 10^{-12})} \text{ ft/sec} = 6.780 \cdot 10^8 \text{ ft/sec}$$

$$C = (1.86 \cdot 10^5 \text{ mi/sec})(5280 \text{ ft/mi}) = 9.821 \cdot 10^8 \text{ ft/sec}$$

EE 420

PULSED TRANSMISSION LINES

Sept 18, 1974

LAB #1

$$\text{so } \frac{v}{c} = \frac{6.780 \cdot 10^8}{9.821 \cdot 10^8} = 0.690 \Rightarrow v = 69\% \text{ OF } c$$

where c = speed of light in a vacuum $\approx$ speed of light in air


2. Define delay constant as the time required for a traveling wave to move a distance of one meter in the cable.

$$D = vt_d \Rightarrow t_d = \frac{1 \text{ m}}{v} = .69 c$$

$$t_d = \frac{1 \text{ m}}{(.69)(3 \cdot 10^8 \text{ m/sec})} = 4.831 \text{ nsec}$$

3. Assume that the length of the cable from "A" to "B", L_{AB} , is 200 meters. Given the conditions in Table 1, what would be the voltage and current waveforms at "A" & at "B" from $t=0$ to $t=7 \mu\text{sec}$

TABLE 1

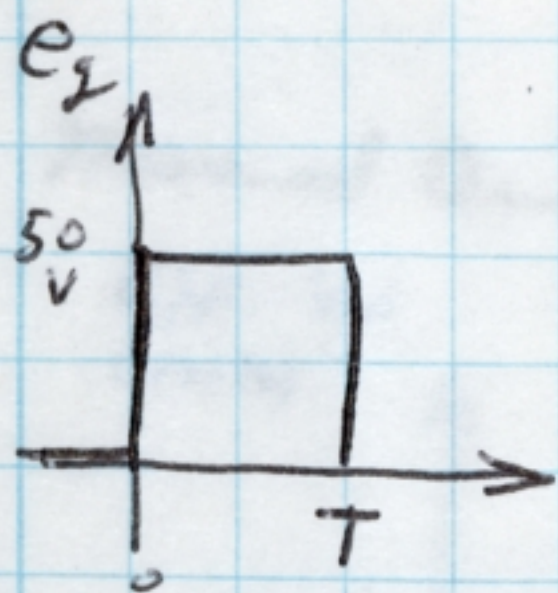

PULSE VOLTAGE, e_g VOLTS	PULSE DURATION, T μSEC	LOAD OHMS
+50	1	50
+50	1	0 (SHORT)
+50	1	OPEN
+50	3	OPEN

With a generator amplitude of 50 V, the voltage which appears at "A" would be given by

$$V_A = \frac{R_o}{R_o + R_g + 100} e_g = \frac{50}{50 + 50 + 100} e_g = .25 e_g = 12.5 \text{ Volts}$$

EE 420

PULSED TRANSMISSION LINES

Sept 18, 1974

EXP. #1

$$v = 1m / 4.831 nsec = 207 m/\mu sec$$



$$K_A = \frac{150-50}{200} = 0.5$$

$$K_B = \frac{50-50}{100} = 0$$



Case 1 : $R_L = 50 \Omega$, $T = 1 \mu sec$, $L_{AB} = 200 m$, $v = 1m / 4.831 nsec$

time interval	V_A^+	V_A^-	I_A^+	I_A^-	V_B^+	V_B^-	I_B^+	I_B^-
0 - 1 μsec	12.5	0	0.25	0	*	*	*	*
0.966 - 1.966 μsec	*	*	*	*	12.5	0	0.25	0
1.933 - 2.933 μsec	0	12.5	0	0	0	0	0	0

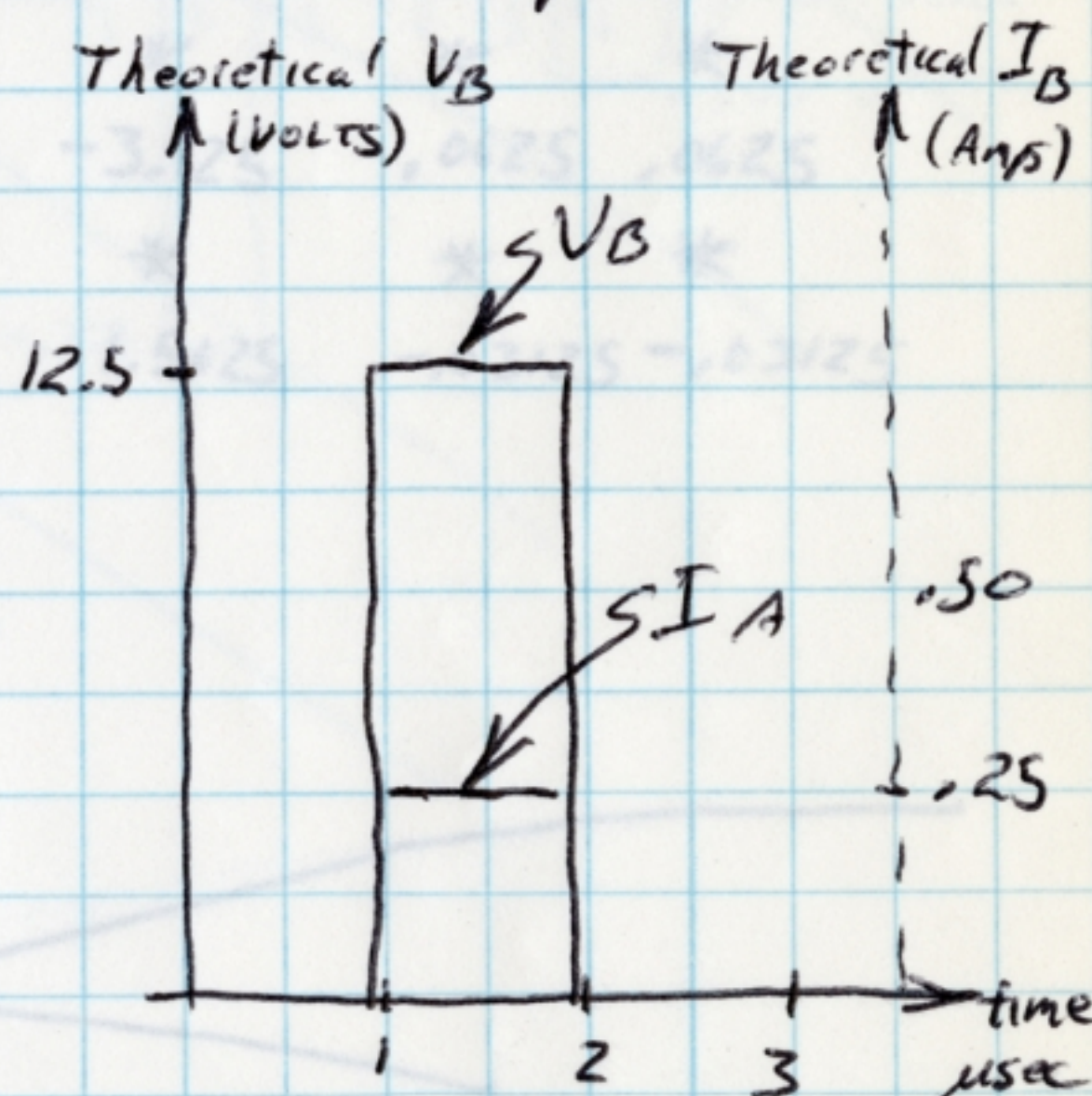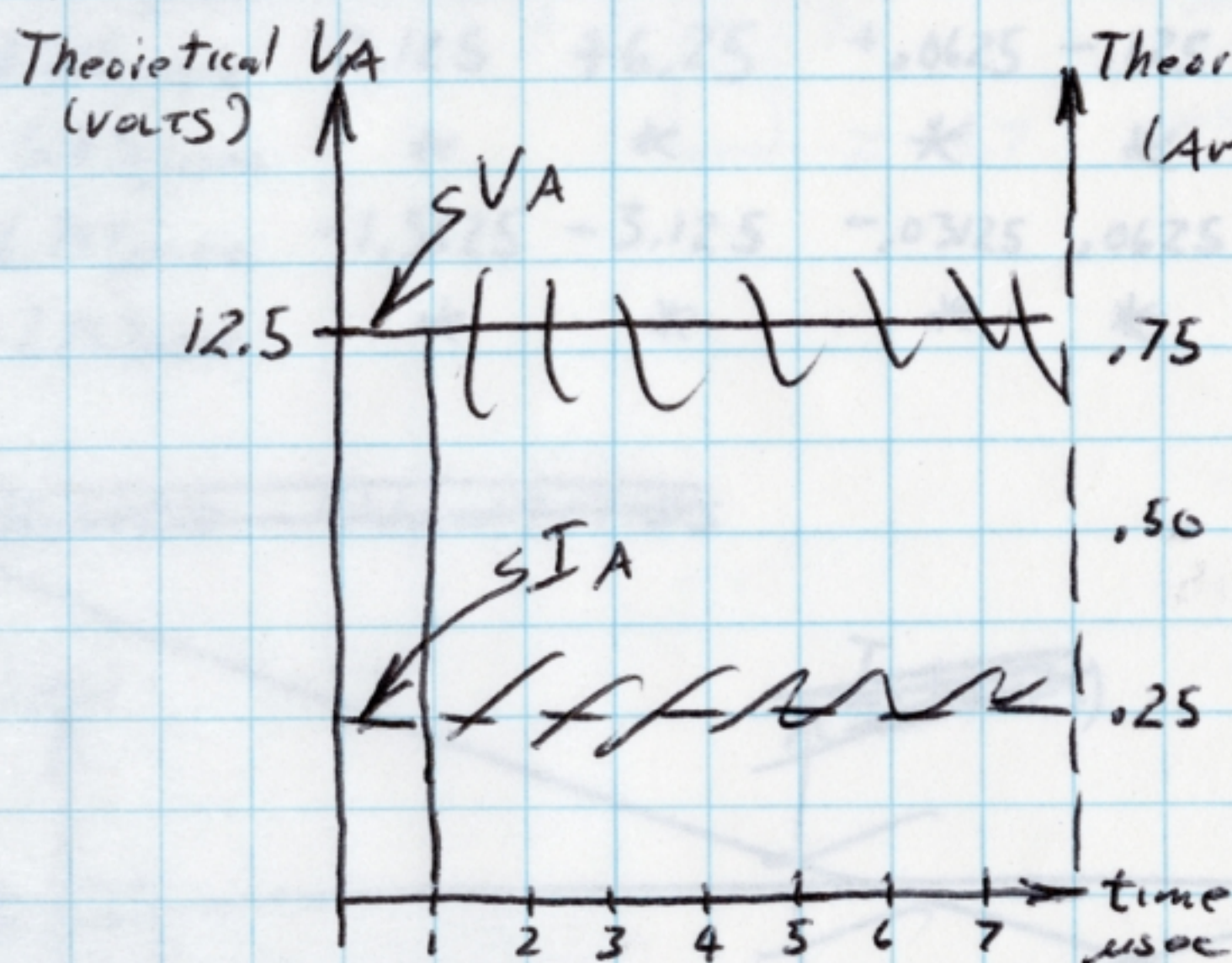When the load is matched to the line, there is no reflection



Measured Quantities

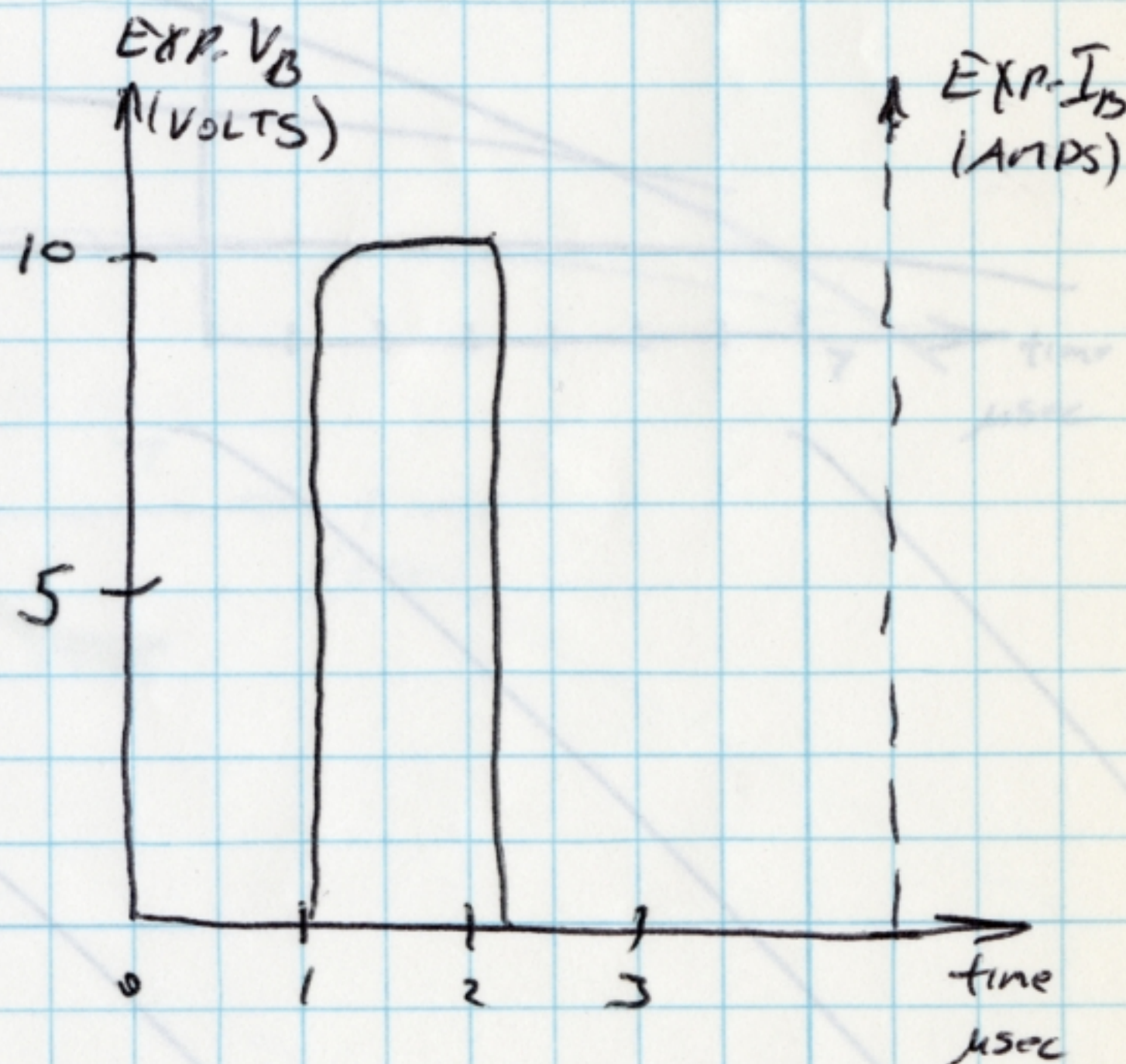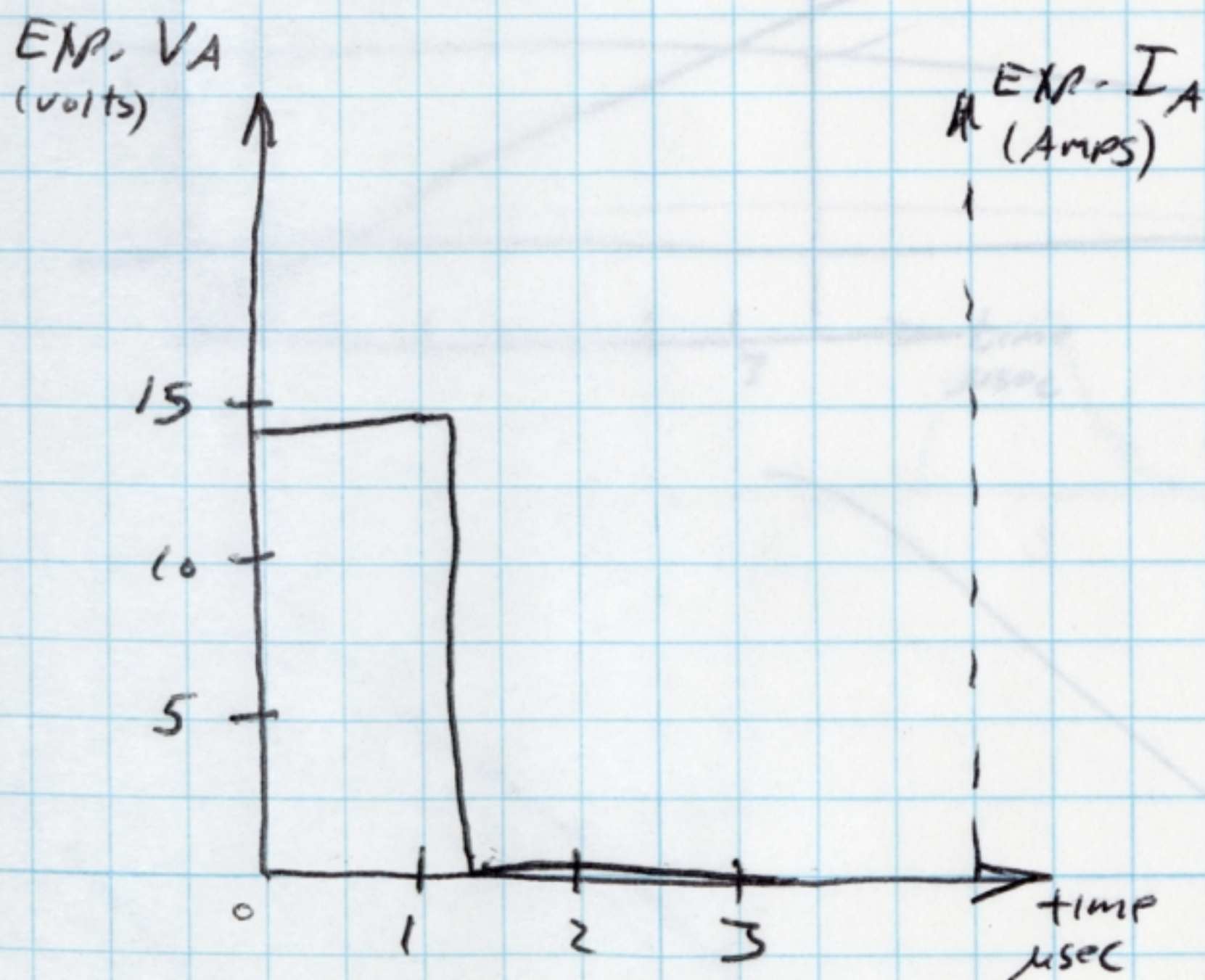

Case 2: $R_L = 0$, $V = 207 \text{ m}/\mu\text{sec}$, $T = 1 \mu\text{sec}$, $L_{AB} = 200 \text{ m}$

$$K_A = \frac{150 - 50}{200} = 0.5$$

$$K_B = \frac{0 - 50}{0 + 50} = -1$$


$$V_A = V_A^+ + V_A^- \quad I_A = I_A^+ + I_A^-$$

$$V_B = V_B^+ + V_B^- \quad I_B = I_B^+ + I_B^-$$

* INDICATES NO CALCULATION MADE



time interval	V_A^+	V_A^-	I_A^+	I_A^-	V_B^+	V_B^-	I_B^+	I_B^-
0 - $1 \mu\text{sec}$	12.5	0	0.25	0	*	*	*	*
0.966 - $1.966 \mu\text{sec}$	*	*	*	*	12.5	-12.5	+0.25	+0.25
1.932 - $2.932 \mu\text{sec}$	-6.25	-12.5	-0.125	+0.25	*	*	*	*
2.899 - $3.899 \mu\text{sec}$	*	*	*	*	-6.25	+6.25	-0.125	-0.125
3.865 - $4.865 \mu\text{sec}$	3.125	+6.25	+0.0625	-0.125	*	*	*	*
4.831 - $5.831 \mu\text{sec}$	*	*	*	*	3.125	-3.125	,0625	,0625
5.797 - $6.797 \mu\text{sec}$	-1.5625	-3.125	-.03125	,0625	*	*	*	*
6.763 - $7.763 \mu\text{sec}$	*	*	*	*	-1.5625	1.5625	-.03125	-.03125

~~CALCULATED~~ QUANTITIES

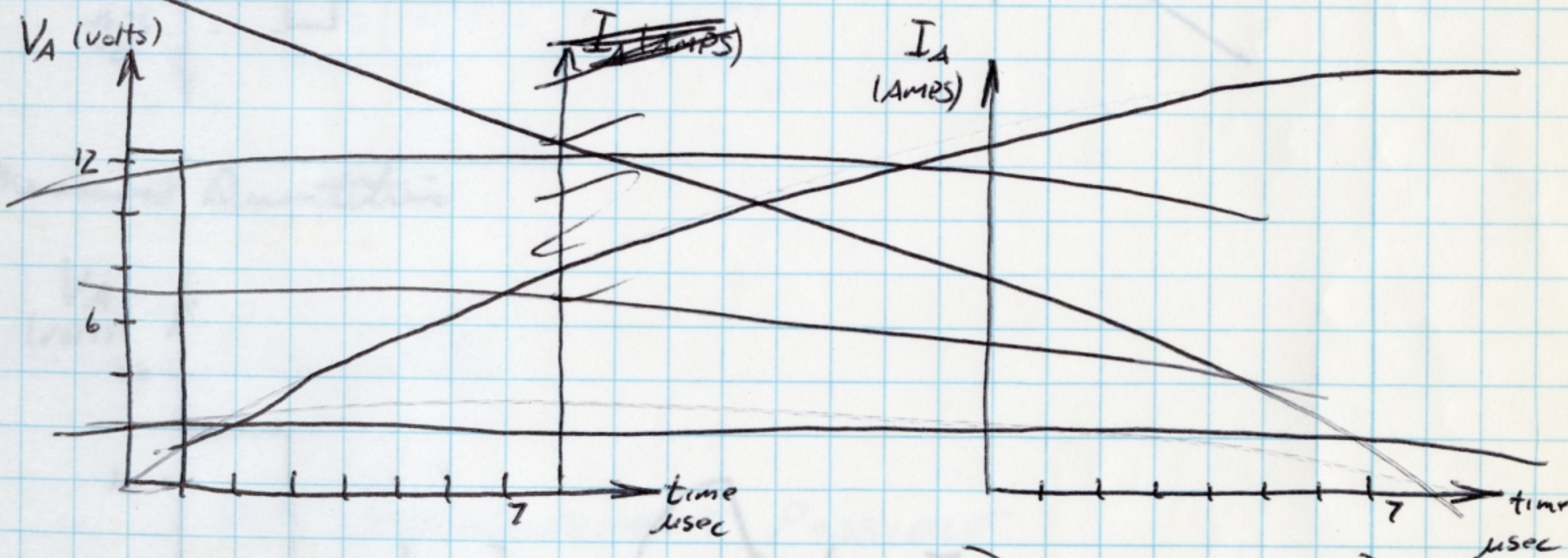


Sept 18, 1974

Calculated Quantities

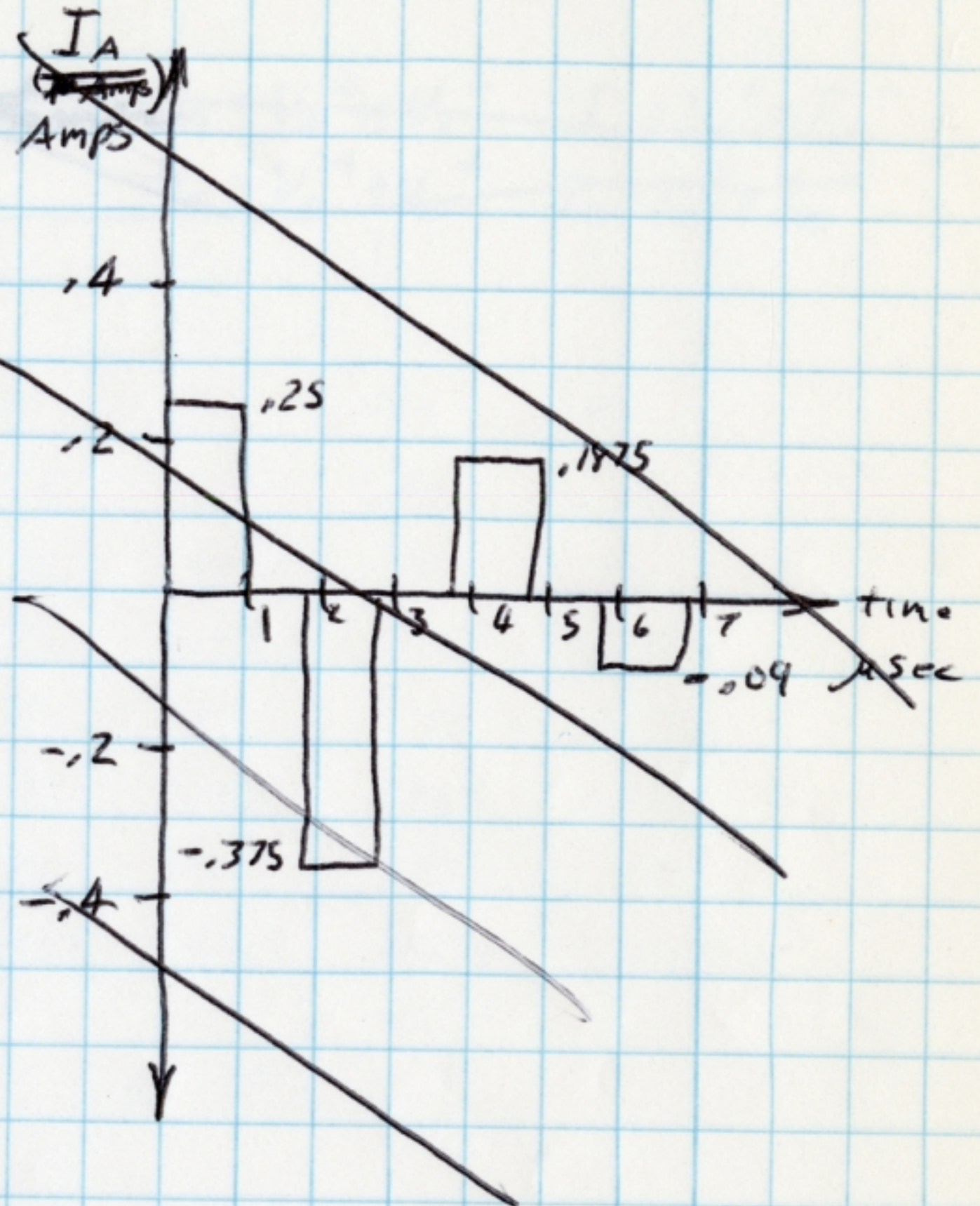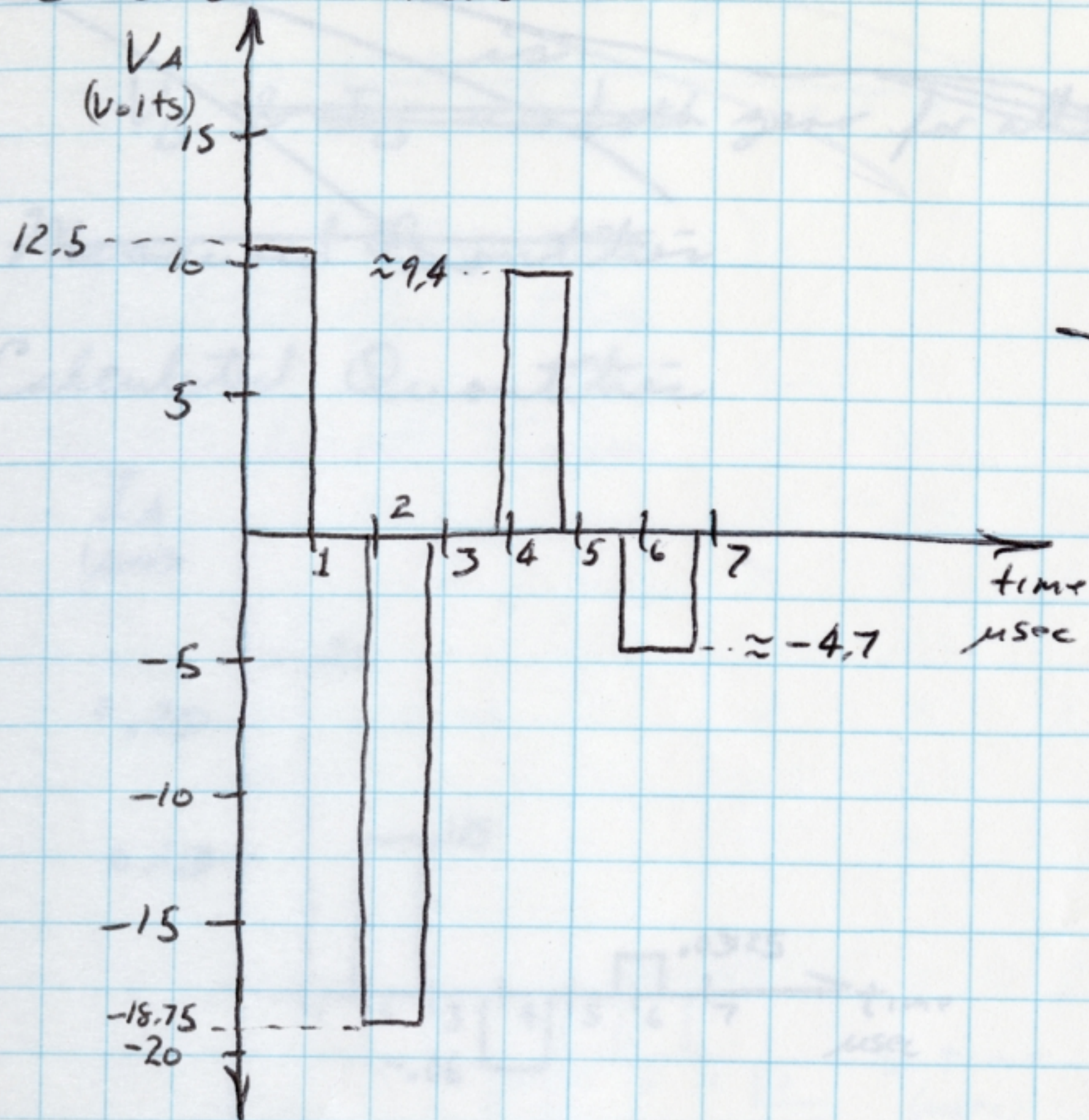

Measured Quantities

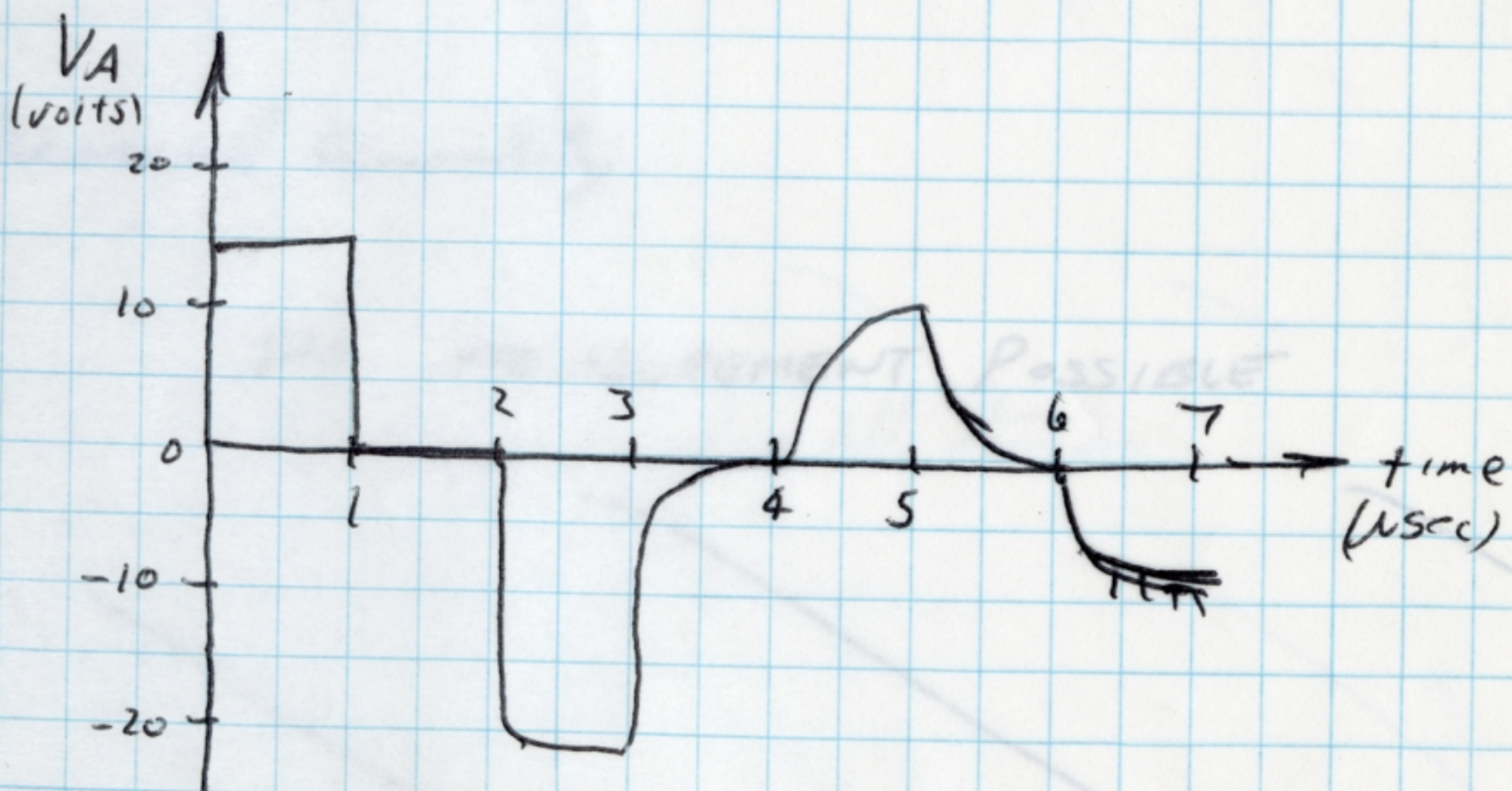

EE 420

PULSED TRANSMISSION LINES

Sept 18, 1974


EXP #1

~~Calculated Quantities~~

is

 ~~V_B & I_B are both zero for all times~~~~Measured Quantities~~

Calculated Quantities

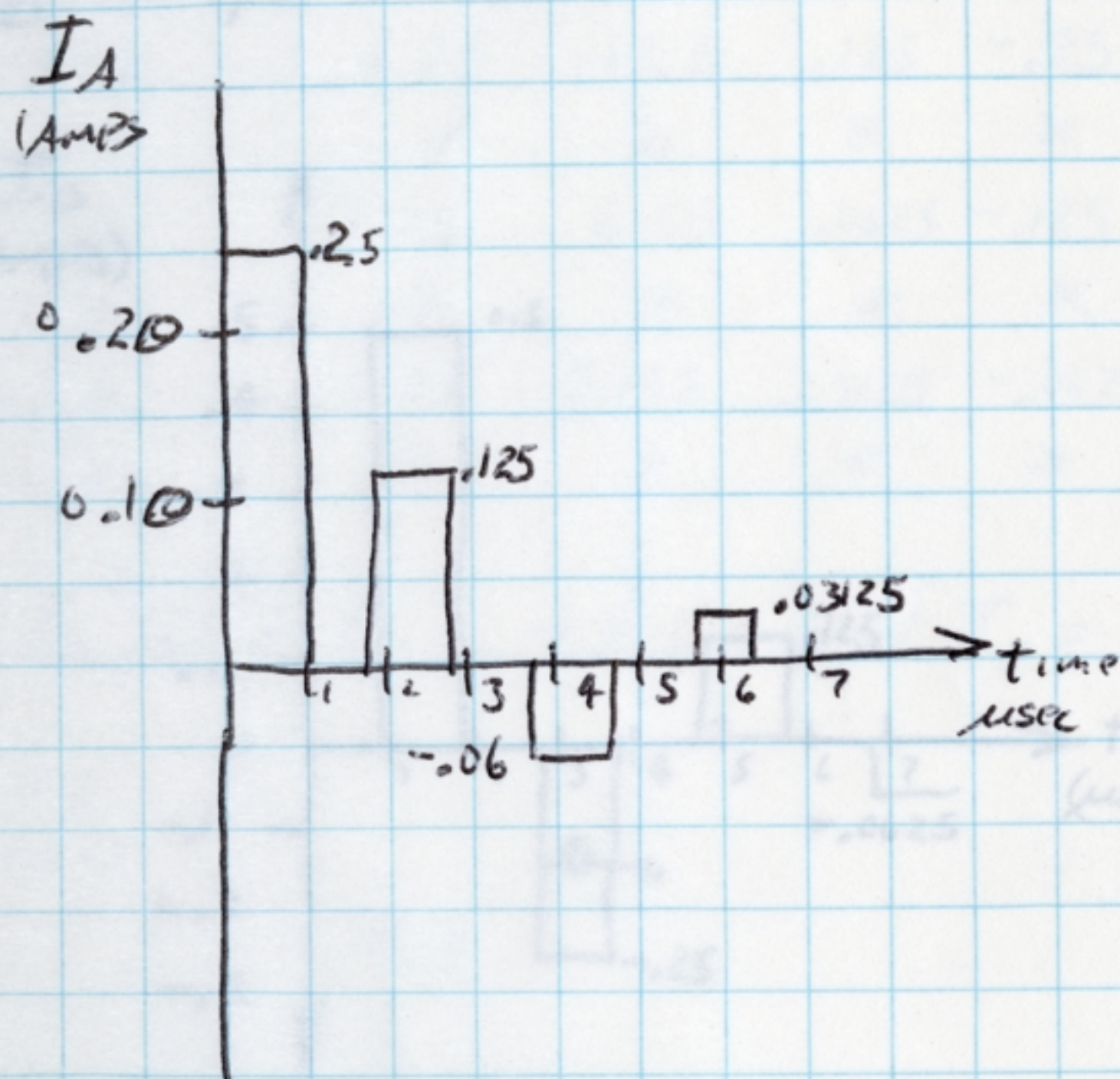

Measured Quantity

NO MEASUREMENT POSSIBLE

EE 420

EXP #1

PULSED TRANSMISSION LINES

Sept 18, 1974

~~Case 3: $R_L = \infty$, $T = 1 \mu\text{sec}$, $V = 207 \text{ mV}$~~

~~$K_A = \frac{150-50}{200} = 0.5$~~

~~$K_B = +1$~~


~~$V_A = V_A^+ + V_A^-$~~

~~$I_A = I_A^+ + I_A^-$~~

~~$V_B = V_B^+ + V_B^-$~~

~~$I_B = I_B^+ + I_B^-$~~

Calculated Quantities

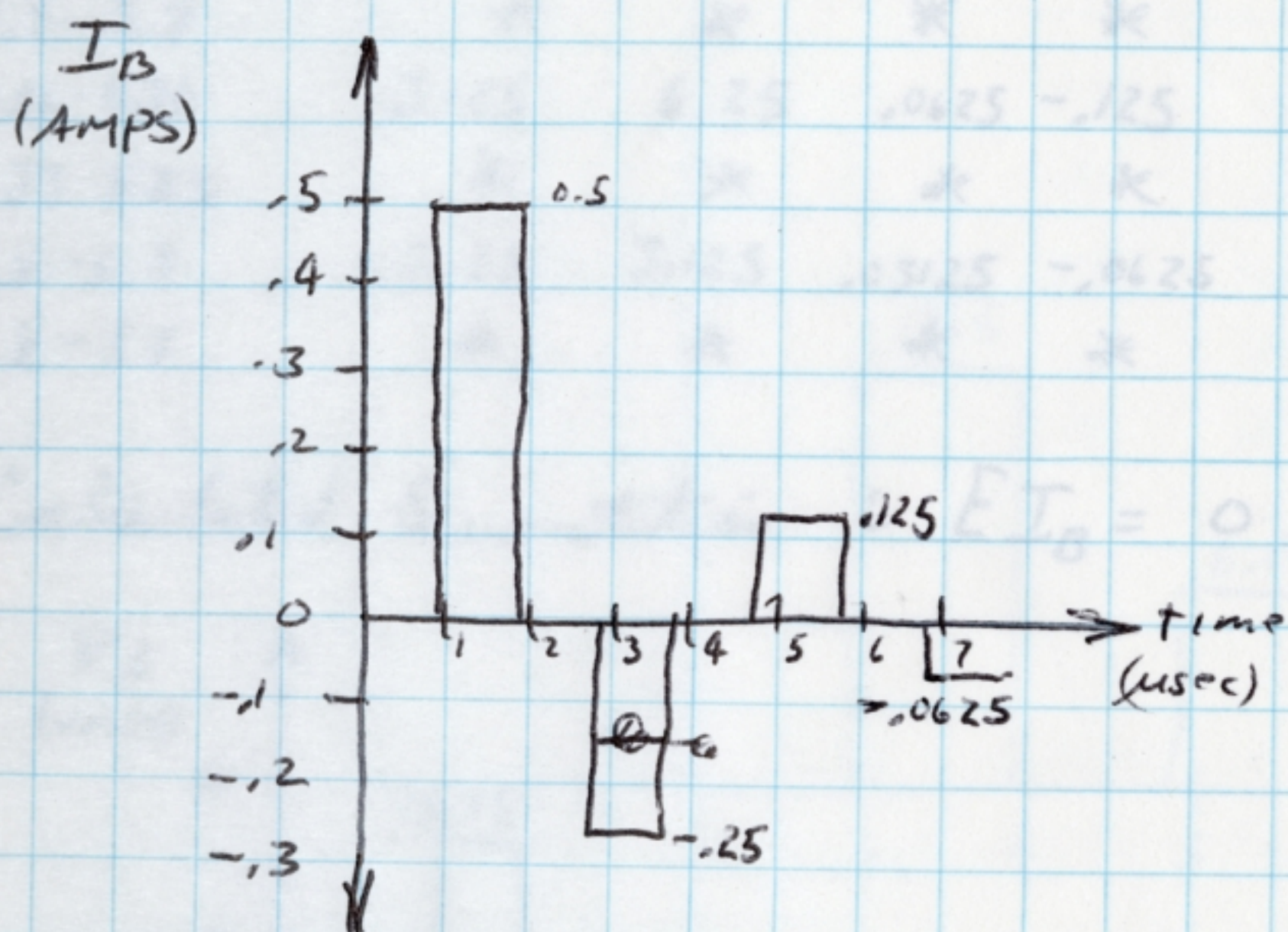 $V_B = 0$ for all times

Measured Quantities

 $V_B = \text{zero for all times}$

EE420
EXP #1


PULSED TRANSMISSION LINES

Sept 18, 1974


Case 3 $R_0 = 50$, $R_L = \infty$ $v = 207 \text{ m}/\mu\text{sec}$ $R_g + 100 = 150$ $T = 1 \mu\text{sec}$
 $K_A = 0.5$ $K_B = +1$ $V = V^+ + V^-$ $I = I^+ + I^-$ $V^- = V^+ K_L$
 $I^- = I^+ (-K_L)$

time interval (μsec)	V_A^+	V_A^-	I_A^+	I_A^-	V_B^+	V_B^-	I_B^+	I_B^-
0-1	12.5	0	0.25	0	*	*	*	*
0.97-1.97	*	*	*	*	12.5	12.5	.25	-.25
1.93-2.93	6.25	12.5	.125	-.25	*	*	*	*
2.9-3.9	*	*	*	*	6.25	6.25	.125	-.125
3.86-4.86	3.125	6.25	.0625	-.125	*	*	*	*
4.83-5.83	*	*	*	*	3.125	3.125	.0625	-.0625
5.8-6.8	1.5625	3.125	.03125	-.0625	*	*	*	*
6.8-7.8	*	*	*	*	1.5625	1.5625	.03125	-.03125

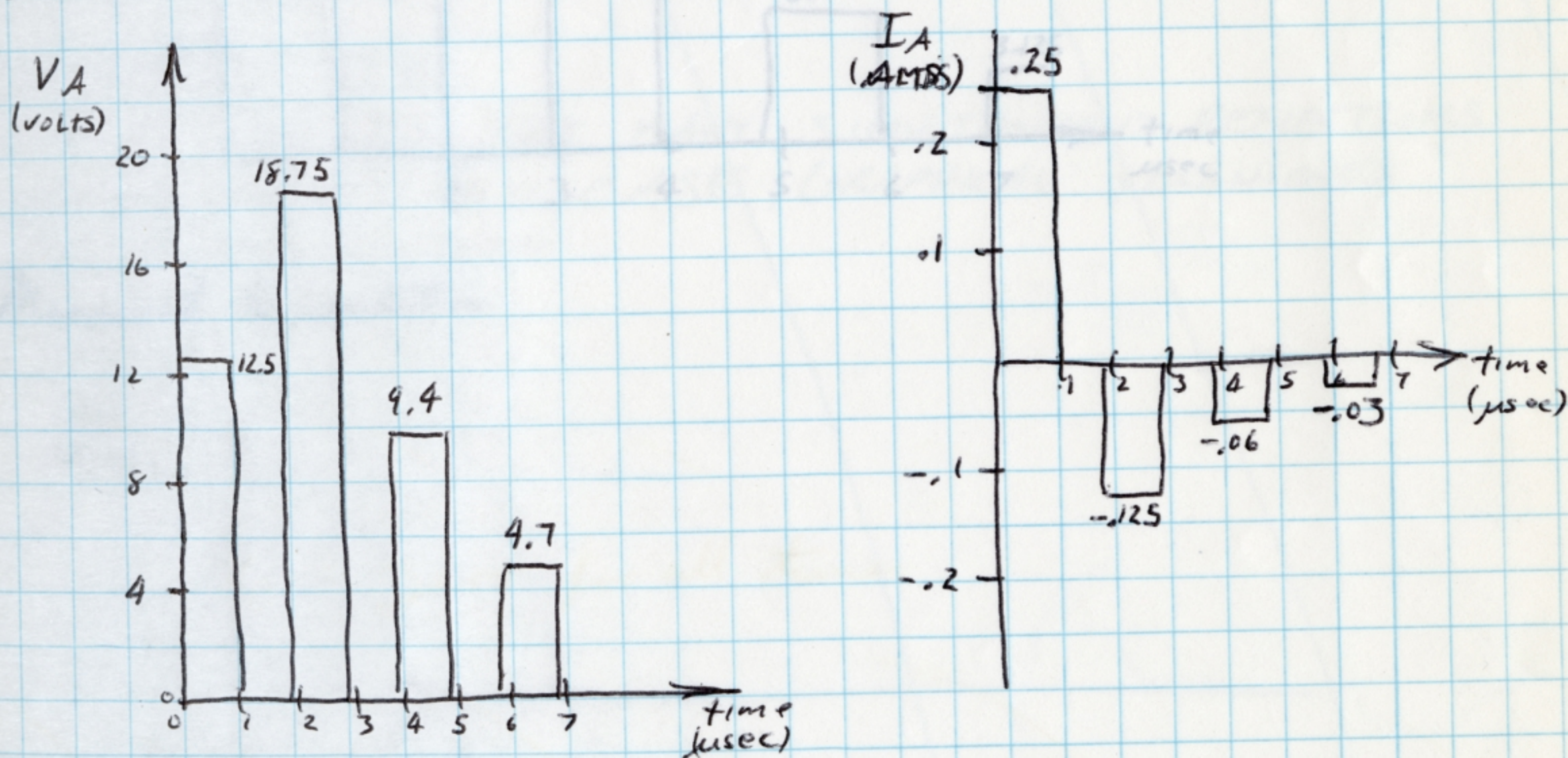Calculated Quantities : $E I_B = 0$ for all times



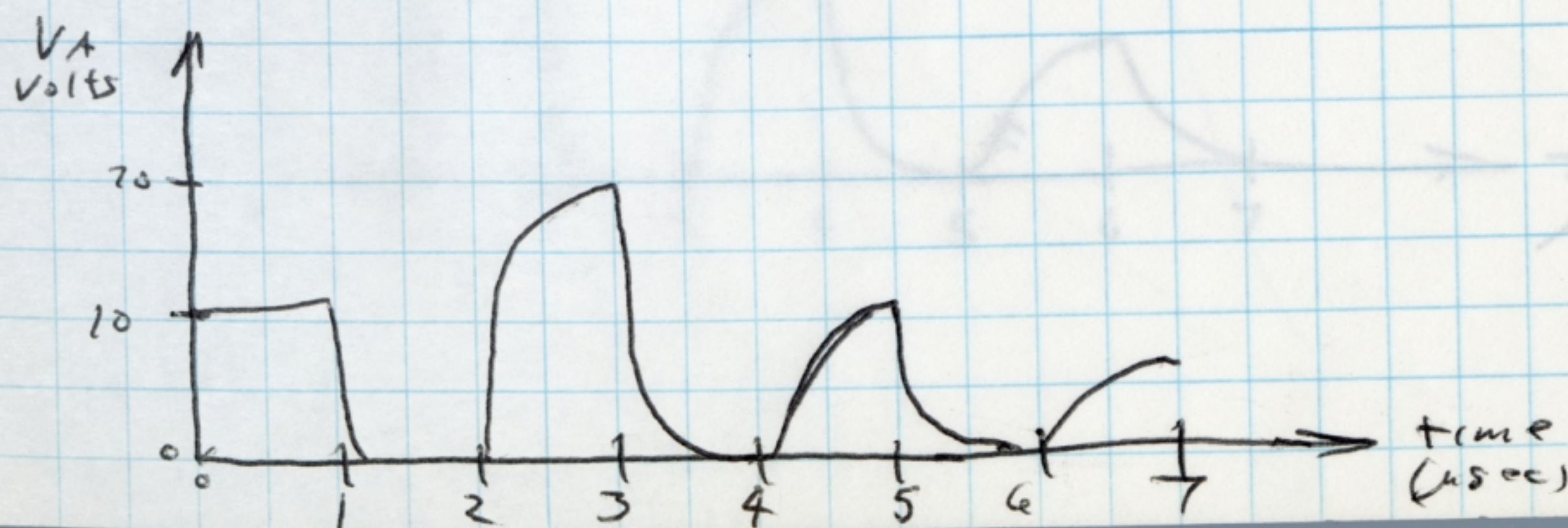Measured Quantities

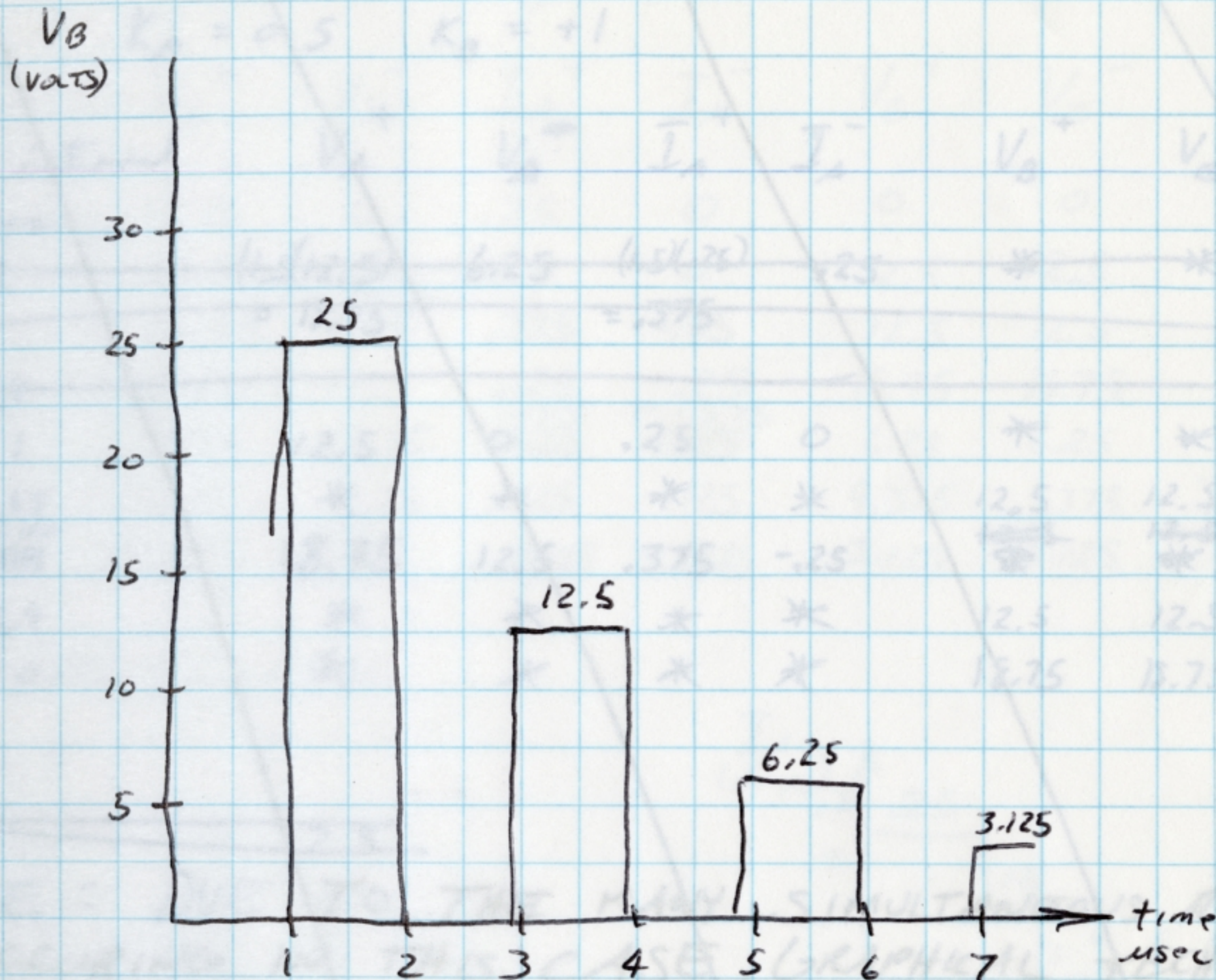


EE 420

PULSED TRANSMISSION LINES

Sept 18, 1974

Exp #1

Calculated Quantities $[I_B = 0 \text{ for all times}]$ 

Measured Quantities

